



**GANDAKI COLLEGE OF  
ENGINEERING AND SCIENCE**



# **Bachelor of Engineering in Computer Engineering**

## **Chapter-2: DC Circuit Analysis**

**By: Asst. Prof. Menaka Karki**

# Contents

1. Application of Kirchhoff's Laws in network solution
  - i. Nodal Analysis
  - ii. Mesh Analysis
2. Superposition theorem
3. Thevenin's theorem
4. Norton's theorem
5. Maximum power transfer theorem

## Objectives of all theorems:

- To find the current flowing
- To find the voltage
- To find the power consumption

# **Application of Kirchhoff's Laws in network solution**

## **Nodal Analysis**

# Application of Kirchhoff's Laws in network solution

## Nodal Analysis

**We solve for finding “Voltage”**

- Find the possible **number of nodes**
- **Assign the variable** at each of the nodes which is unknown
- Select **the reference node**, generally ground/ common point
- For each of the unknown, form **an equation based on KCL**
- If there are **voltage sources between two unknown junction**, join the two nodes as **super node**. The currents of the two nodes are combined in a single equation and a new equation for the voltage is formed.
- **Solve** the equations for each **unknown voltage**.

# Application of Kirchhoff's Laws in network solution


## Nodal Analysis Conditions

1. Circuit containing **only current source**
2. Circuit containing **voltage source in addition to current source**
  - i. **Voltage source transformable into current source**
  - ii. **Voltage source not transformable into current source**
    - a. **Voltage source involving reference node**
    - b. **Voltage source not involving reference node**

# 1. Circuit containing only current source
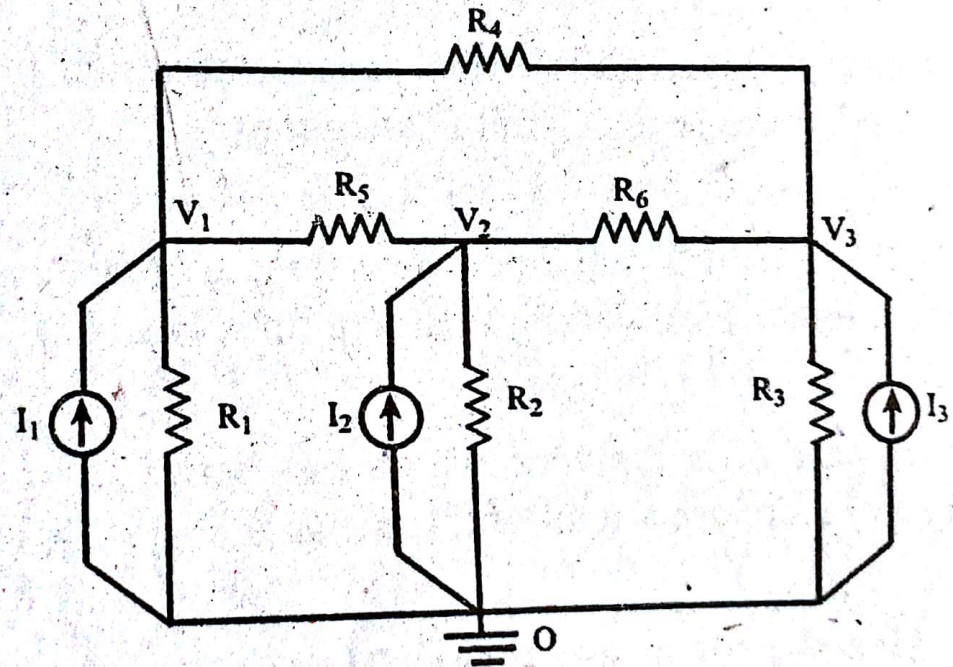
## Nodal Analysis

- Find the possible number of **nodes**
- Select the **reference node**, generally ground/ common point
- **Assign the variable** at each of the nodes which is unknown
- For each of the unknown, form an **equation** based on KCL
- Identify if there are any **super node**. Then combine two nodes in a single equation and a new equation for the voltage is formed.
- **Solve** the equations for each unknown voltage.



Applying KCL at node 1,

$$\frac{V_1 - 0}{R_1} + \frac{V_1 - V_2}{R_5} + \frac{V_1 - V_3}{R_4} = I_1$$

Applying KCL at node 3,




$$\frac{V_3 - 0}{R_3} + \frac{V_3 - V_2}{R_6} + \frac{V_3 - V_1}{R_4} = I_3$$

Applying KCL at node 2,

$$\frac{V_2 - 0}{R_2} + \frac{V_2 - V_1}{R_5} + \frac{V_2 - V_3}{R_6} = I_2$$
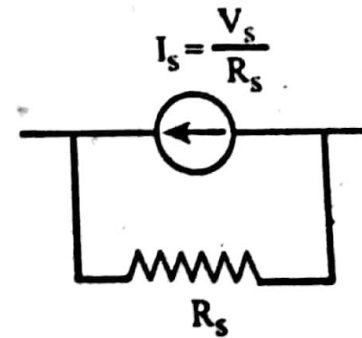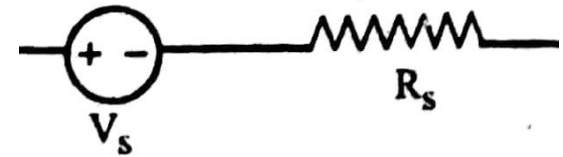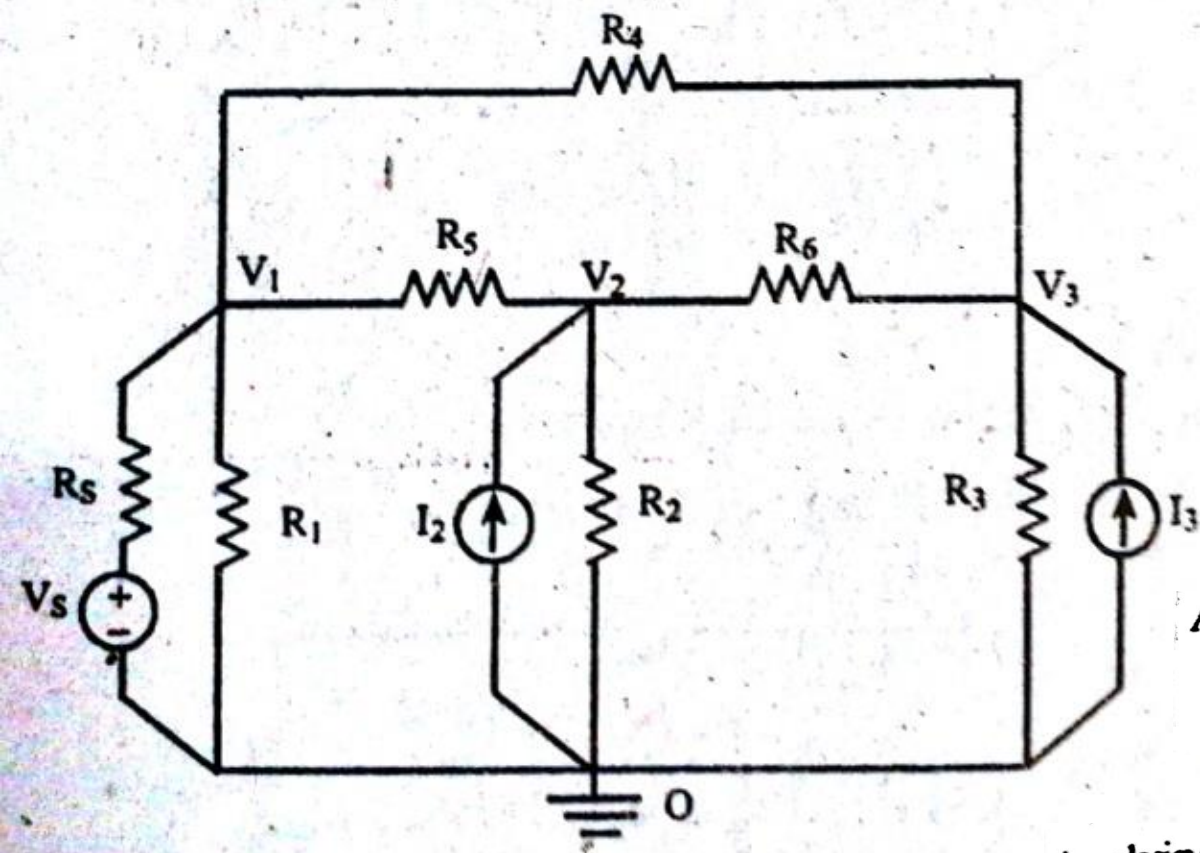
## 2. Circuit containing voltage source in addition to current source

Voltage source transformable into current source



Applying KCL at node 2,

$$\frac{V_2 - 0}{R_2} + \frac{V_2 - V_1}{R_5} + \frac{V_2 - V_3}{R_6} = I_2.$$

Applying KCL at node 3,

$$\frac{V_3 - 0}{R_3} + \frac{V_3 - V_2}{R_6} + \frac{V_3 - V_1}{R_4} = I_3.$$


Applying KCL at node 1,

$$\frac{V_1 - V_2}{R_5} + \frac{V_1 - V_3}{R_4} + \frac{V_1 - V_s}{R_s} + \frac{V_1 - 0}{R_1} = 0.$$


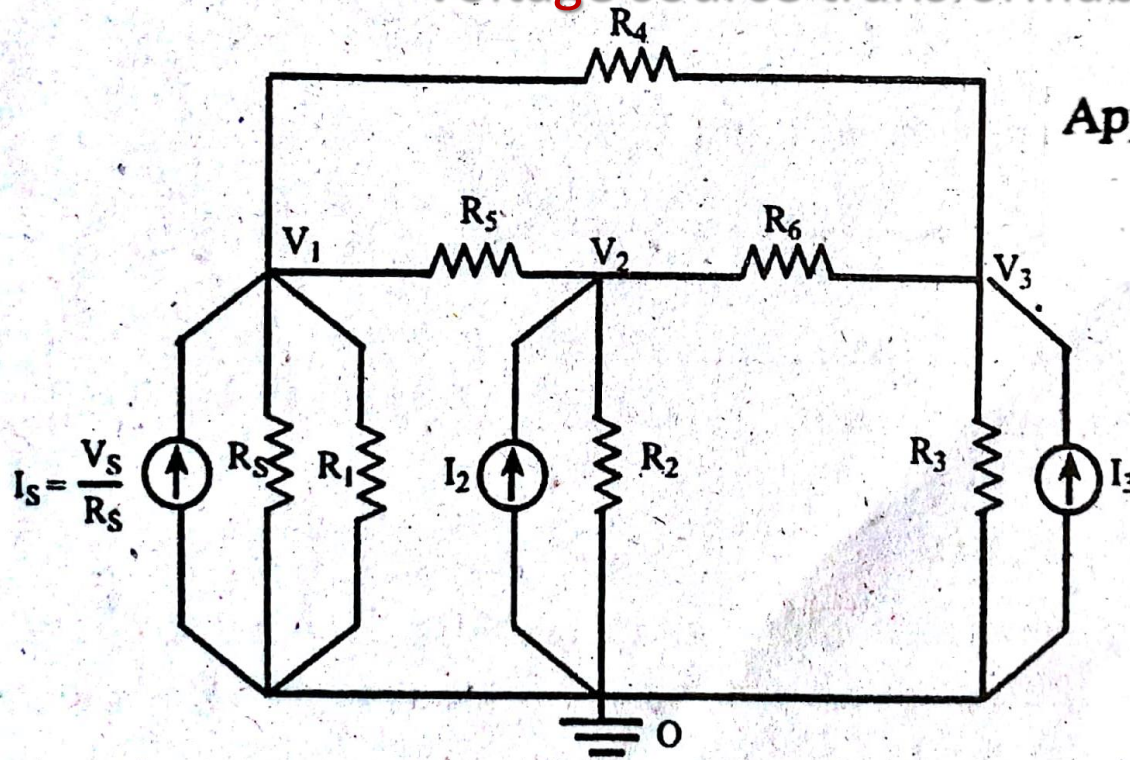
## 2. Circuit containing voltage source in addition to current source

Voltage source transformable into current source





Applying KCL at node 1,

$$\frac{V_1 - V_2}{R_5} + \frac{V_1 - V_3}{R_4} + \frac{V_1 - 0}{R_s} + \frac{V_1 - 0}{R_1} = \frac{V_s}{R_s}$$

Applying KCL at node 2,
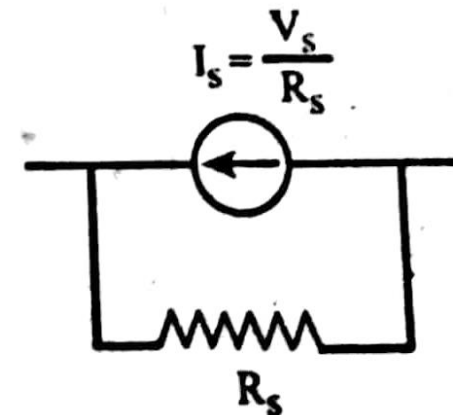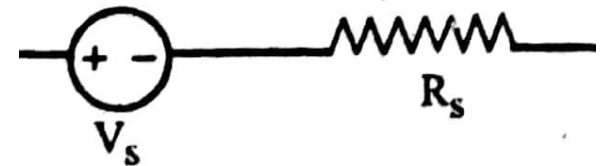
$$\frac{V_2 - 0}{R_2} + \frac{V_2 - V_1}{R_5} + \frac{V_2 - V_3}{R_6} = I_2$$



Applying KCL at node 3,


$$\frac{V_3 - 0}{R_3} + \frac{V_3 - V_2}{R_6} + \frac{V_3 - V_1}{R_4} = I_3$$



## 2. Circuit containing voltage source in addition to current source

Voltage source not transformable into current source

Voltage source involving reference node

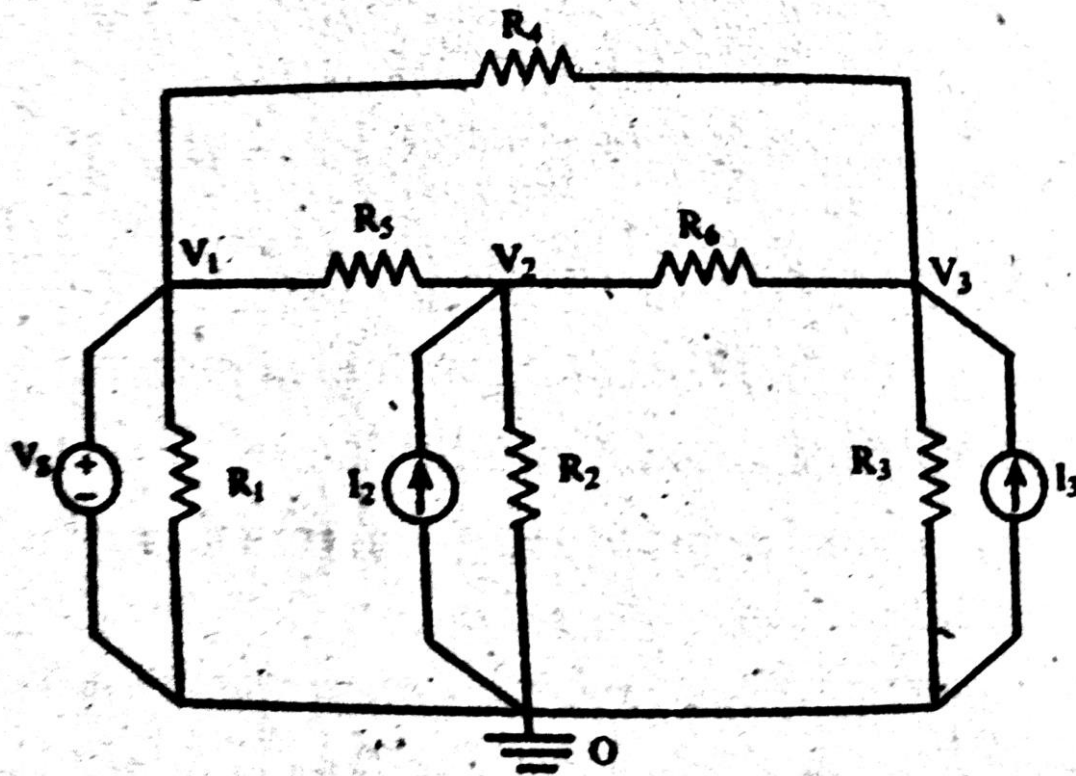

Here,  $V_s = V_1 - 0$   
or,  $V_1 = V_s$  .....

Applying KCL at node 2,

$$\frac{V_2 - 0}{R_2} + \frac{V_2 - V_1}{R_5} + \frac{V_2 - V_3}{R_6} = I_2$$


Applying KCL at node 3,

$$\frac{V_3 - 0}{R_3} + \frac{V_3 - V_2}{R_6} + \frac{V_3 - V_1}{R_4} = I_3$$
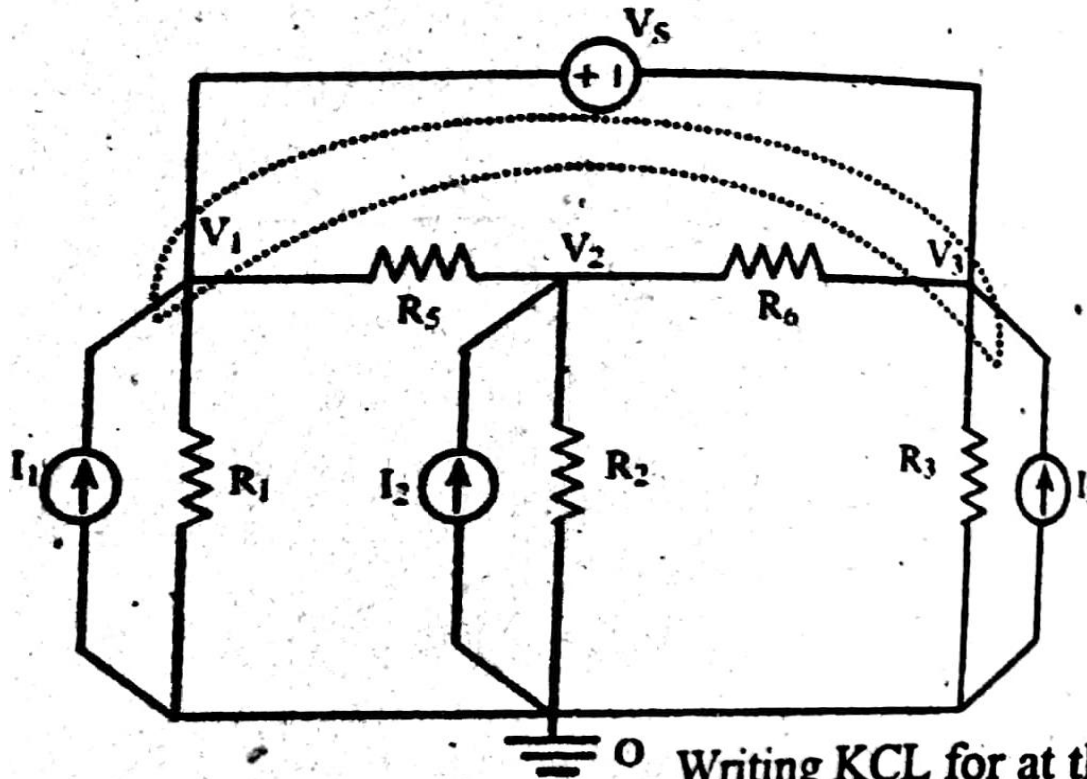
## 2. Circuit containing voltage source in addition to current source

Voltage source not transformable into current source

Voltage source not involving reference node



Super nodes

$$V_1 - V_3 = V_s$$

Writing KCL for at the supernode 1 and 3,

$$\frac{V_1 - 0}{R_1} + \frac{V_1 - V_2}{R_5} + \frac{V_3 - 0}{R_3} + \frac{V_3 - V_2}{R_6} = I_1 + I_3$$




Applying KCL at node 2,

$$\frac{V_2 - 0}{R_2} + \frac{V_2 - V_1}{R_5} + \frac{V_2 - V_3}{R_6} = I_2$$

# Classwork

**Q. Use nodal analysis to find the current through 3 ohm resistor in the circuit.**

**Ans:  $2/3$  A**

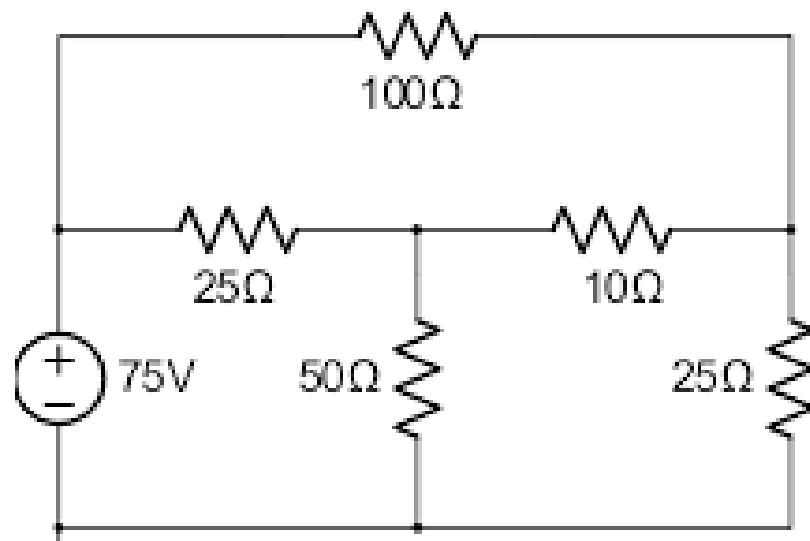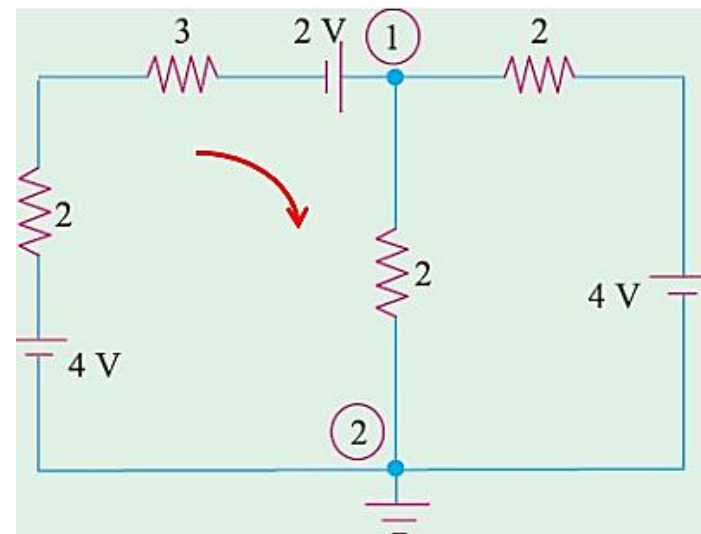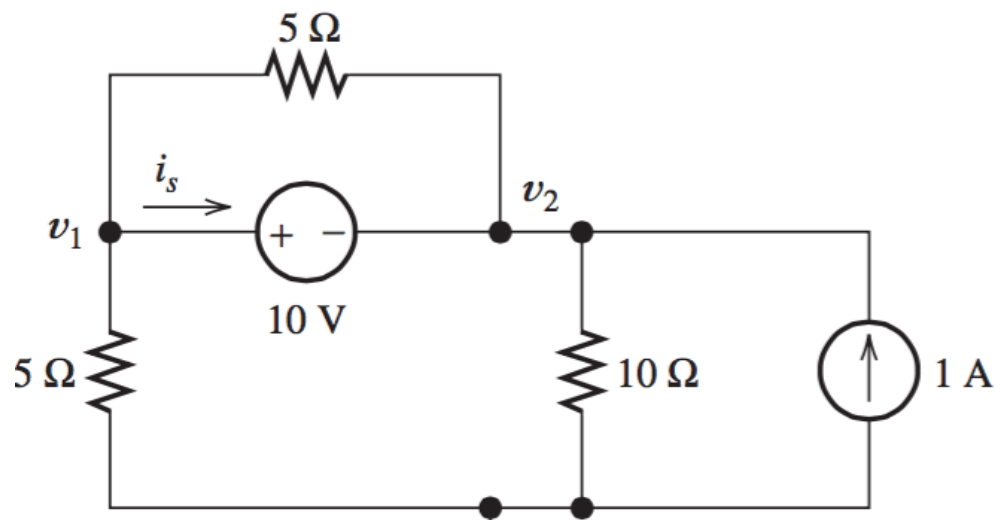

# **Application of Kirchhoff's Laws in network solution**

## **Mesh Analysis**

# Application of Kirchhoff's Laws in network solution

## Mesh Analysis

- Find the possible **number of mesh**.
- Assume the smallest number of **mesh currents** so that at least one mesh current links every element. As a matter of convenience, all mesh currents can be assumed to have clockwise direction
- For each mesh, write **KVL equation**. When **more than one mesh current flows** through an element the **algebraic sum of currents** should be used. The algebraic sum of mesh currents may be the sum or the difference of the currents flowing through the element depending on the **direction of mesh currents**.
- **Solve** the above equations and from the mesh currents find the **branch currents**.

**We solve for finding “Current”**

# Application of Kirchhoff's Laws in network solution


## Mesh Analysis

1. Circuit containing **only voltage sources**
2. Circuit containing **current source + Voltage source**
  - i. Current source transformable into voltage source
  - ii. Current source not transformable into voltage source
    - a. Current source present in the **perimeter of any individual loop**
    - b. Current source present in the **common branch of any two loops**



# Mesh Analysis
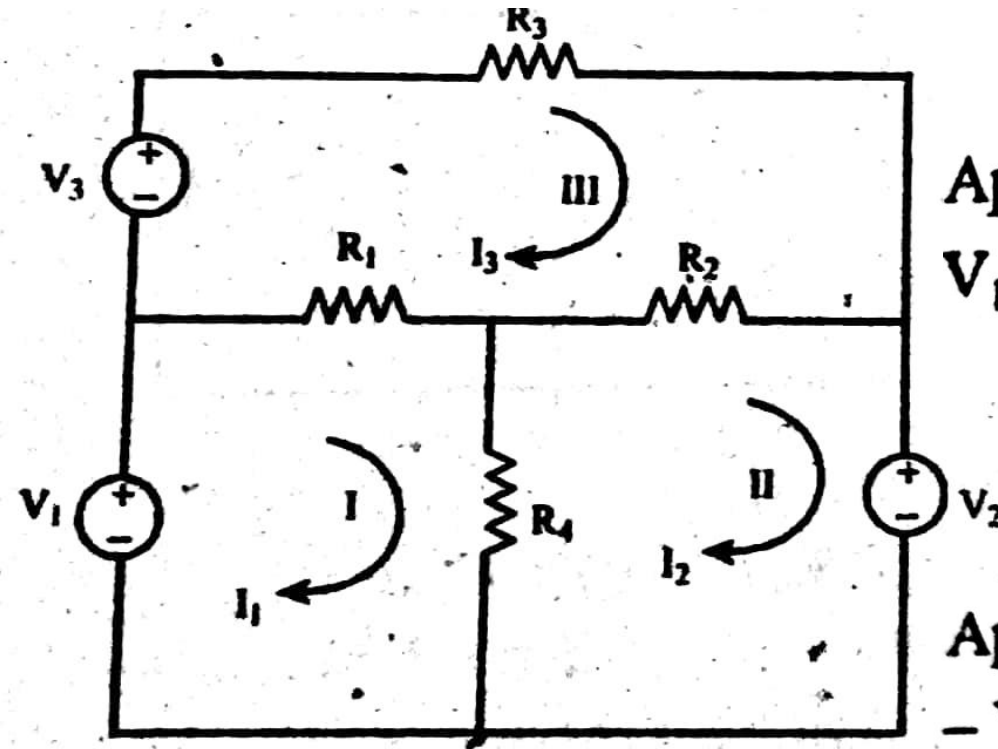
## 1. Circuit containing only voltage sources




Applying KVL to the loop I, we get  
 $V_1 - (I_1 - I_3)R_1 - (I_1 - I_2)R_4 = 0$

Applying KVL to the loop II, we get  
 $-V_2 - (I_2 - I_1)R_4 - (I_2 - I_3)R_2 = 0$

Applying KVL to the loop III, we get  
 $V_3 - I_3R_3 - (I_3 - I_2)R_2 - (I_3 - I_1)R_1 = 0$
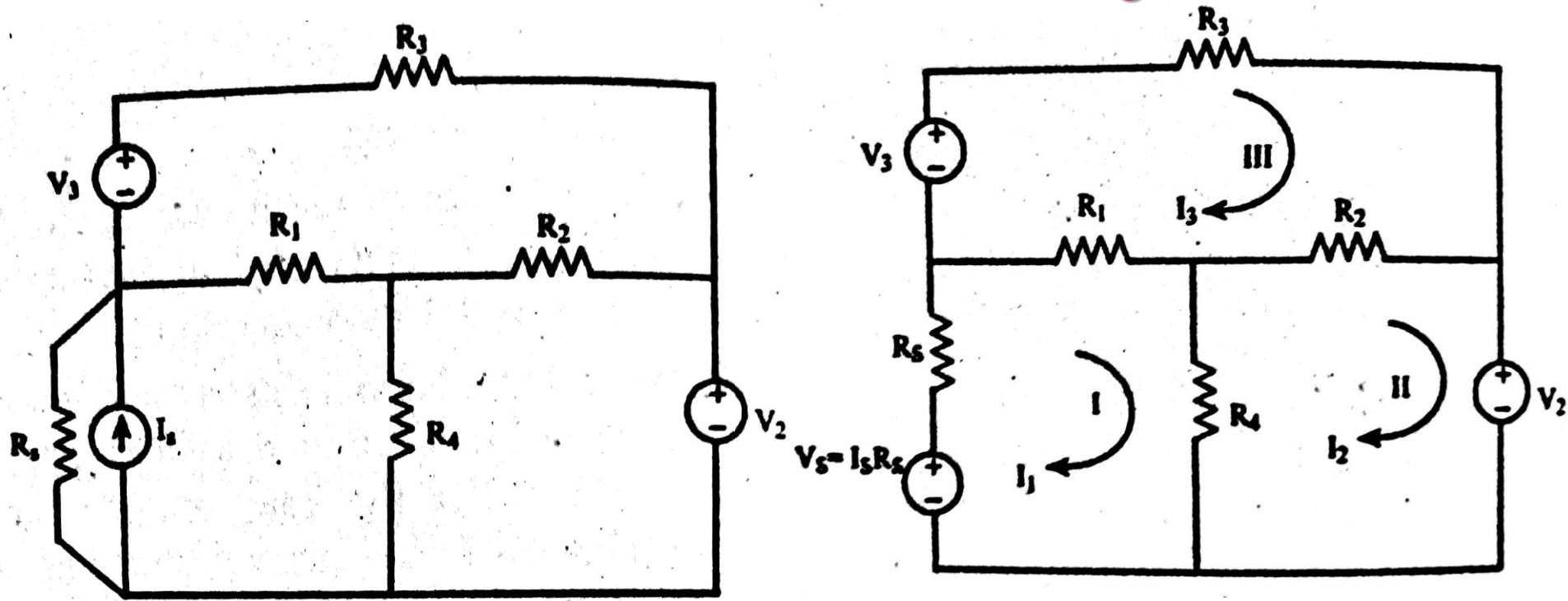
## 2. Circuit containing current source + Voltage source

Current source transformable into voltage source



Applying KVL to the loop I, we get

$$I_s R_s - I_1 R_s - R_1 (I_1 - I_3) - R_4 (I_1 - I_2) = 0$$

Applying KVL to the loop II, we get


$$-V_2 - (I_2 - I_1)R_4 - (I_2 - I_3)R_2 = 0$$

Applying KVL to the loop III, we get

$$V_3 - I_3 R_3 - (I_3 - I_2)R_2 - (I_3 - I_1)R_1 = 0$$

## 2. Current source not transformable into voltage source

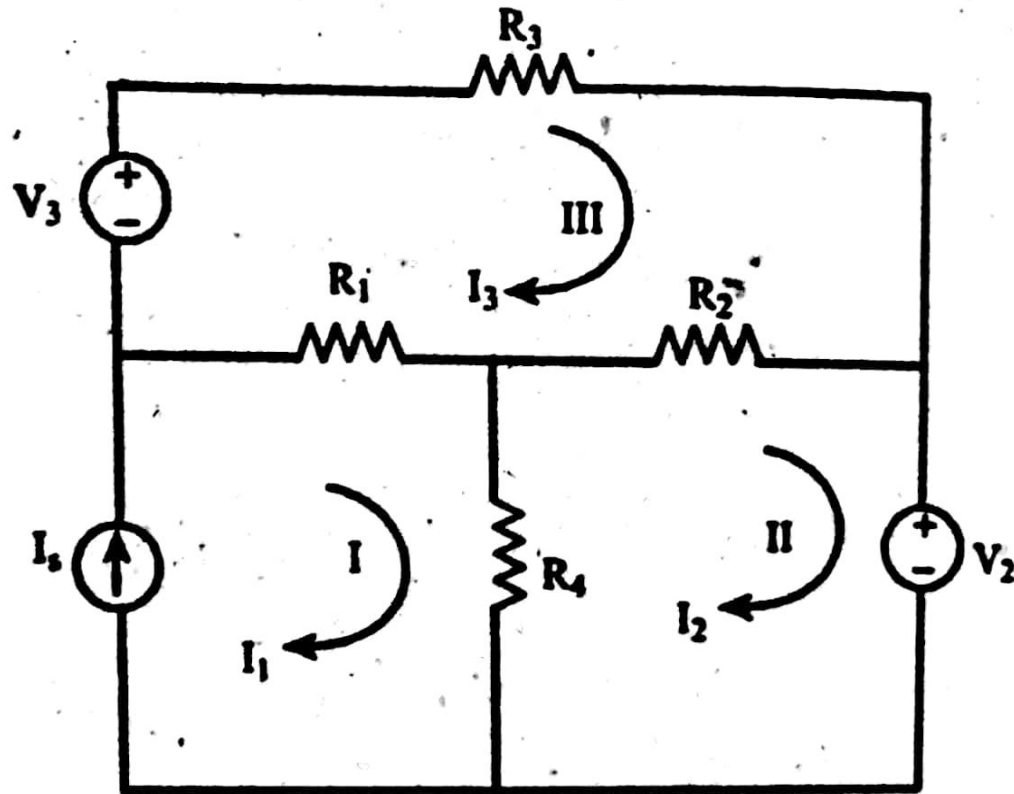- i. Current source present in the perimeter of any individual loop



$$I_1 = I_s \dots$$

Applying KVL to the loop II , we get

$$-V_2 - (I_2 - I_1)R_4 - (I_2 - I_3)R_2 = 0$$

Applying KVL to the loop III, we get


$$V_3 - I_3R_3 - (I_3 - I_2)R_2 - (I_3 - I_1)R_1 = 0$$

## 2. Current source not transformable into voltage source

ii. Current source present in the common branch of any two loops

Applying KVL to the loop II, we get  
 $-V_2 - (I_2 - I_1)R_4 - (I_2 - I_3)R_2 = 0$

$$I_3 - I_1 = I_S \dots$$

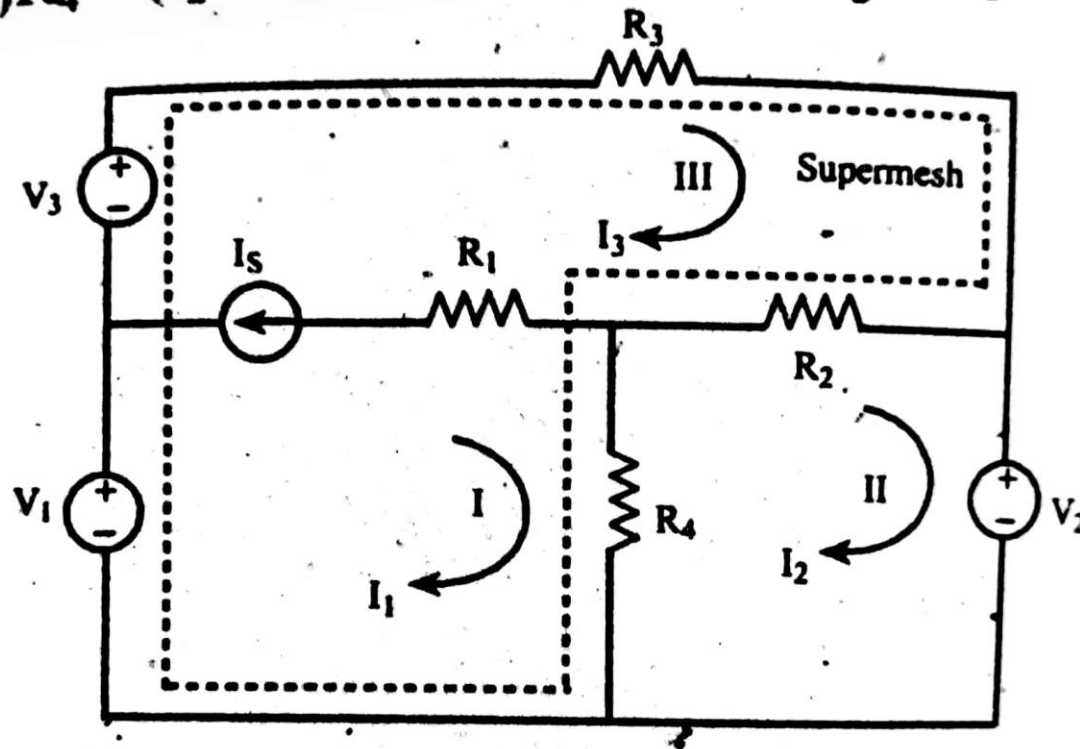


Applying KVL for supermesh I and III, we get



$$V_3 - I_3 R_3 - R_2 (I_3 - I_2) - R_4 (I_1 - I_2) + V_1 = 0$$
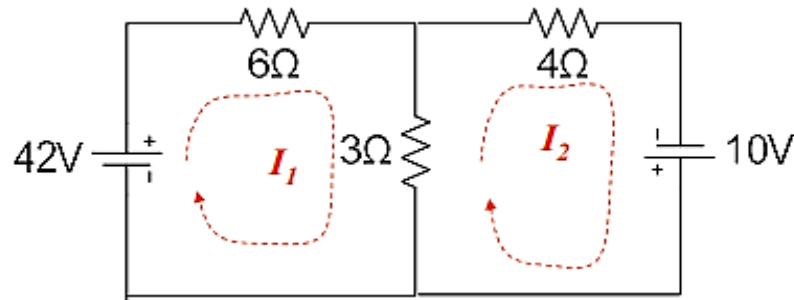
# Classwork

Q. Use mesh analysis to find the power consumption in the resistor 3 ohm?



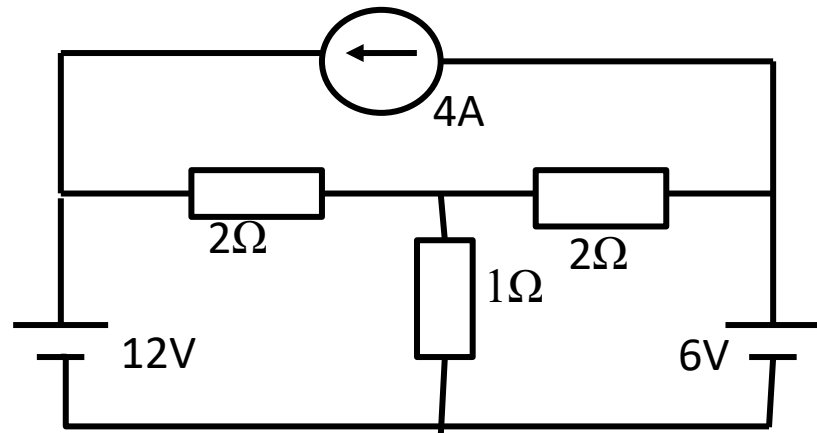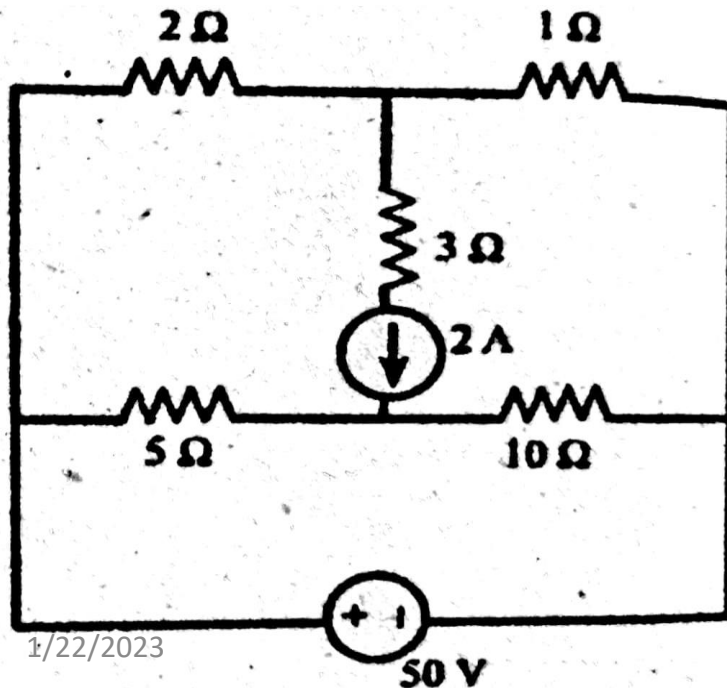Q. Find the current through 1 ohm resistor using mesh/ loop analysis.



Q. Determine the current in the 5 ohm resistor in the network shown, using loop formulation method.