

Write short notes on: (Any two)

- Role of electricity in modern society.
- Losses in transformer.
- Quality Factor and Band Width.

Level: Bachelor

Semester: Spring

Year : 2014

Programme: BE

Full Marks: 100

Course: Basic Electrical Engineering

Pass Marks: 45


Time : 3hrs.

Candidates are required to give their answers in their own words as far as practicable.


The figures in the margin indicate full marks.

Attempt all the questions.

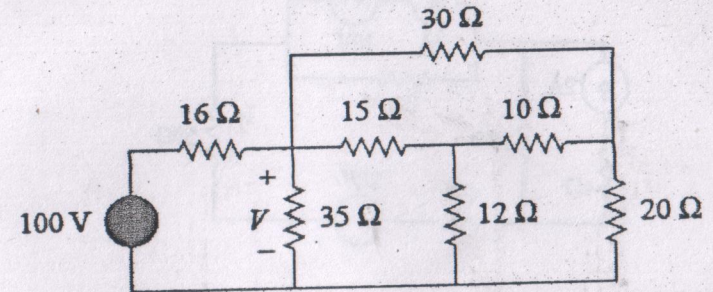- Obtain the equivalent resistance and use it to find source current for the circuit shown below. Also find V . 7



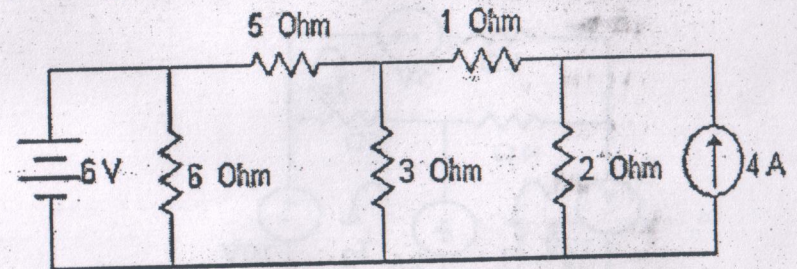- Applying Superposition theorem, calculate the current in 5Ω resistor of circuit given below. 8



- Calculate the power absorbed/ delivered by 6V source for the network shown in Fig. using nodal analysis. 7