

Level: Bachelor

Semester: Fall

Year : 2020

Programme: BE

Full Marks: 100

Course: Electronic Devices and Circuits


Pass Marks: 45

Time : 3hrs.


Candidates are required to give their answers in their own words as far as practicable.

The figures in the margin indicate full marks.

Attempt all the questions.

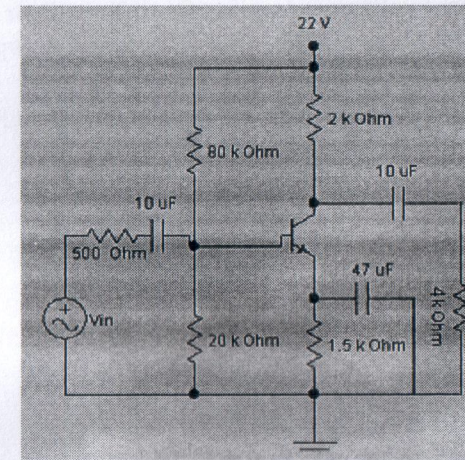


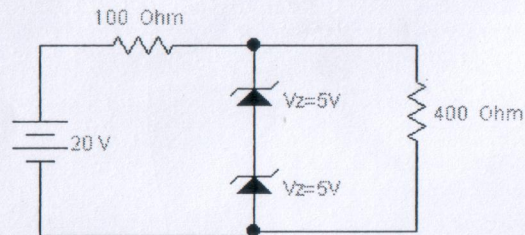1. a) What happens when a forward biased diode is suddenly reverse biased? Explain with necessary diagrams. If reverse saturation current of diode is 5nA at 35°C, find reverse saturation current at 235°C. 8
- b) For the circuit given below, find the output voltage, current flowing through a zener diode, and voltage drop across a series resistance, and power dissipated across the zener diode. 7



2. a) Explain thermal instability and thermal runaway. Define stability factor and find stability Factor for any one configuration of a transistor. 7
- b) For the BJT common emitter circuit shown below, determine the operating point and locate it in the load line. Assume $\beta = 100$. 8

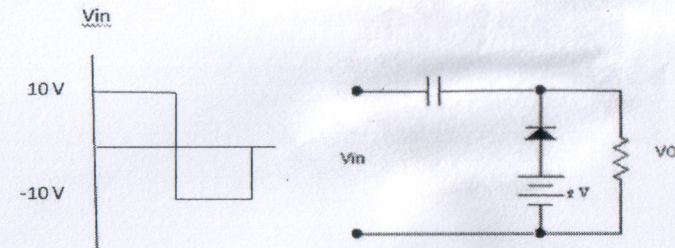3. a) Sketch output waveform for given circuit assuming silicon diode. 8



- b) What is pinch-off voltage? Design a self bias NJFET circuit operating at 15mA and 10V. Given $I_{DSS}=25mA$, $V_p=-4V$ and $V_{DD}=25V$. Also find the transconductance. 7
4. a) A CE amplifier transistor having $h_{ie}=8k\Omega$, $h_{re}=3.6 \times 10^{-4}$, $h_{fe}=25\mu A/V$. Determine A_i , A_v , Z_{in} and Z_o of the amplifier while $Z_L=15K\Omega$ and $R_S=500\Omega$. 8
- b) Why cascading is necessary? Find the gain of n-stage cascaded amplifiers. 7
5. a) What do you mean by power amplifier? Show that the maximum possible efficiency of transformer coupled load class A power amplifier is 50%. 7
- b) What are positive and negative feedback? Negative feedback extends the bandwidth. Explain it, with necessary derivations. 8