

Level: Bachelor
 Programme: BE
 Course: Basic Electrical Engineering

Semester: Spring


Year : 2013
 Full Marks: 100
 Pass Marks: 45
 Time : 3hrs.

Candidates are required to give their answers in their own words as far as practicable.


The figures in the margin indicate full marks.

Attempt all the questions.

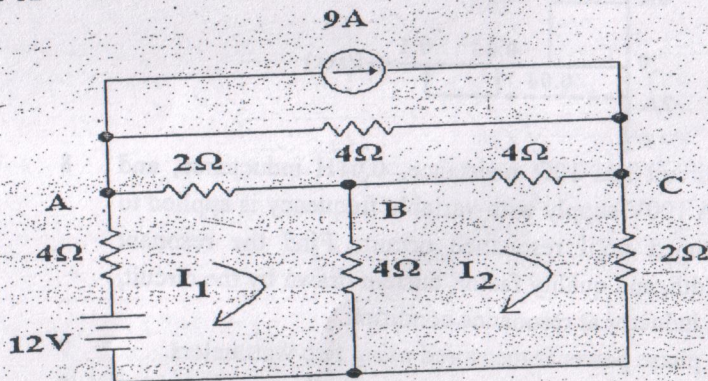
1. a) Draw a typical single line diagram for the transmission and distribution of three phase power and explain why transformer is needed to transfer power over long distance? 7
- b) A resistance wire 10 m long and cross sectional area 10 mm^2 at 0°C passes a current of 10 A when connected to dc supply of 200 volts. Calculate: 8
 - i. Resistivity of the material
 - ii. Current which will flow through the wire when the temperature rises to 50°C . given $\alpha_0 = 0.0003$ per degree centigrade.
2. a) Use nodal analysis to determine the voltage across BC and the current in the 12-V as shown in figure below. 8



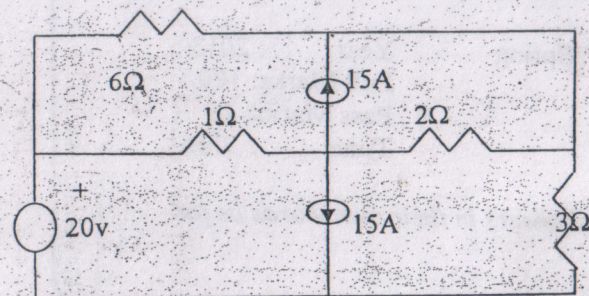
- b) Use superposition theorem to calculate the current through 3Ω of the ckt shown in fig below. 7



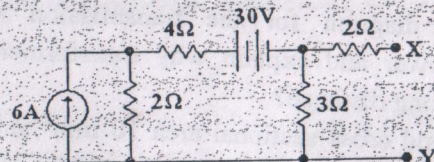3. a) State and explain Norton's theorem. Find the Norton's equivalent for the network to the left of terminals X-Y in the figure shown below. 7



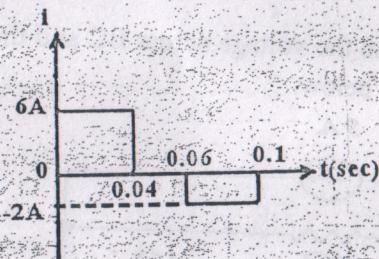- b) A varying current with a periodic waveform as shown in figure below flows through an 8Ω resistor. Determine the 8
- average value
 - rms value
 - heat dissipated in 5 minute.



4. a) A series R-L-C circuit has 10Ω resistance, 0.01H inductance, and $100\mu\text{F}$ capacitor. A 100V supply with variable frequency is applied to this circuit and tuned until resonance occurs. Find the resonant frequency, bandwidth, and quality factor, current drawn by the circuit, and voltage across inductor at resonance condition. 8
- b) Explain how three phase power is measured using two wattmeters. 7
5. a) Three equal impedances having resistance 8Ω and inductive resistance 6Ω are connected in delta and connected to 230V , 3-phase 8

wire $3\phi\text{Y}$ (wye connected) source. Then calculate

- Phase and line current of load
 - Power factor
 - Power consumed
- b) A 25KVA , $400/200\text{V}$, 1ϕ transformer has high voltage winding resistance and reactance are 0.2Ω and 0.5Ω respectively. The values of low voltage are 0.6Ω and 0.8Ω respectively. Calculate the equivalent resistance, reactance and impedance referred to 7
- LV side
 - HV side.
6. a) Explain operating principle of 3ϕ Induction motor. 8
- b) A 220V dc shunt motor runs with 1000 rpm with an armature current of 40A . The resistance of armature is 0.5Ω . Calculate the value of resistance to be connected in series so that the speed drops to 600rpm . 7
7. Write short notes on: (Any Two) 2x5
- Ideal and practical sources.
 - Power factor and its significance.
 - Losses in rotating machines.